

741/Transistor Amplifier

I don't claim credit for the design of this circuit as I found it on an Indian Blog (<http://www.homemade-circuits.com/2012/04/make-this-mini-hi-fi-ipod-amplifier.html>). I have tweaked it a bit and designed a PCB.

I'm amazed by how well it works, especially give the reputation 741s have for being no good for audio.

